

WT - Exp - 3

KUNAL PUNJABI 43
MANAV PUNJABI 44
HITESH ROHRA 46

Div: D15A

Project Name: Smoke and Fire Detection System

Aim:

To develop an automated system using Arduino that detects the presence of smoke and fire, triggering an alert mechanism to enhance safety and prevent fire hazards.

Introduction:

Fire hazards pose a serious risk in both residential and industrial environments. Traditional fire detection systems often rely on human intervention, leading to delayed responses and increased damage. This project aims to build a real-time smoke and fire detection system using an Arduino UNO, flame and smoke sensors (MQ2), and an alert mechanism that includes a buzzer and an LCD display. The system enhances safety by providing immediate alerts upon detecting hazardous conditions, making it a reliable and efficient solution for fire prevention and early warning systems.

The system works by continuously monitoring the environment for signs of smoke and fire. The flame sensor detects infrared radiation from fire, while the MQ2 smoke sensor identifies harmful gases and smoke particles in the air. When the sensors detect smoke or fire, the Arduino processes the data and triggers an alert through a buzzer and displays the warning on the LCD screen.

Objectives:

- **Real-time Fire and Smoke Detection:** Implement a system that continuously monitors the surroundings for potential fire hazards.
- **Automatic Alert Mechanism:** Trigger a buzzer and display warning messages when fire or smoke is detected.
- **Compact and Cost-Effective Design:** Ensure the system is easy to implement in homes, offices, and industries with minimal cost.

Challenges:

- **Sensor Sensitivity:** The accuracy of flame and smoke detection can be affected by environmental factors such as lighting conditions and air movement.
- **False Alarms:** Cooking smoke or steam may trigger false alerts, requiring calibration of sensors.
- **Power Supply:** Ensuring an uninterrupted power source for continuous monitoring is crucial.

Solution Approach:

1. **Smoke and Fire Detection:** The MQ2 sensor detects smoke levels, while the flame sensor identifies fire presence.
2. **Data Processing:** The Arduino UNO processes input from sensors and determines whether a fire hazard is present.
3. **Alert Activation:** If smoke or fire is detected, the buzzer sounds an alarm, and the LCD displays a warning message.
4. **User Notification:** The system can be further enhanced by integrating wireless communication to send alerts to users remotely.

Scope:

- **Residential Safety:** Prevents fire hazards in homes by providing early detection.
- **Industrial Applications:** Enhances fire safety in factories and warehouses.
- **Public Places:** Can be used in offices, malls, and schools for fire prevention.

Advantages:


- **Early Detection and Prevention:** Helps minimize fire-related damages by providing immediate alerts.
- **Automation Reduces Human Effort:** Operates without manual intervention, ensuring continuous monitoring.
- **Cost-Effective and Scalable:** Uses readily available components, making it easy to implement and expand.
- **Portable and Compact Design:** Can be installed in various locations without occupying much space.



Conclusion:


Conclusion:


The Arduino-based smoke and fire detection system offers a reliable, cost-effective, and efficient way to enhance fire safety. By integrating MQ2 and flame sensors with an alert mechanism, the project ensures real-time detection and response to fire hazards. This system is suitable for various applications, including homes, industries, and public buildings, making it a valuable tool for fire prevention and safety management.

Components:

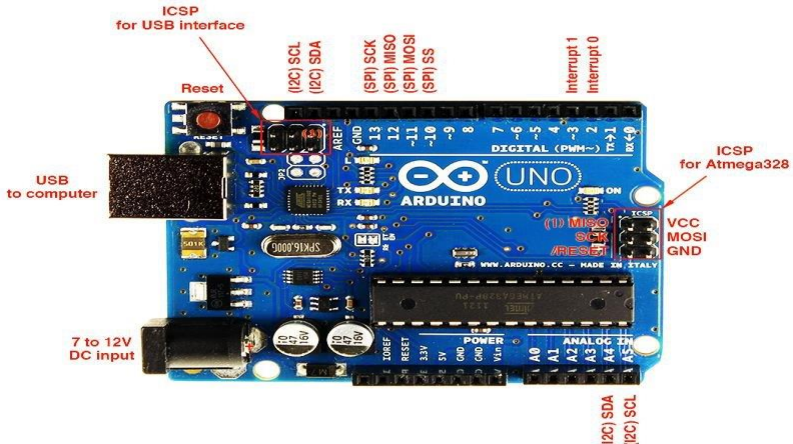Sr no.	Description	Image
1.	Arduino UNO A microcontroller board based on the ATmega328P, used to process data from sensors and control the alert mechanisms, such as the buzzer and LCD display.	 A photograph of an Arduino UNO microcontroller board. Red arrows point to various components and pins, labeled with text: 'ICSP for USB interface' points to the USB connector; 'Reset' points to the reset button; 'USB to computer' points to the USB Type-B port; '7 to 12V DC input' points to the DC power jack; 'ICSP for Atmega328' points to the ICSP header; 'VCC MOSI GND' points to the ICSP pins; 'Interrupt 1 Interrupt 0' points to digital pins 2 and 3; and '(I2C) SDA (I2C) SCL' points to digital pins 4 and 5. Other labels include '(SPI) SCK (SPI) MISO (SPI) MOSI (SPI) SS', 'DIGITAL (PWM~)', 'ARDUINO', and 'UNO'.
2.	16x2 LCD Display A small screen that displays real-time status updates, such as warnings when smoke or fire is detected.	 A photograph of a 16x2 LCD display module. The screen is green and displays the text 'This is a 2x16 line LCD Display' in a pixelated font. The module has a green PCB with gold-colored pins along the top and bottom edges.

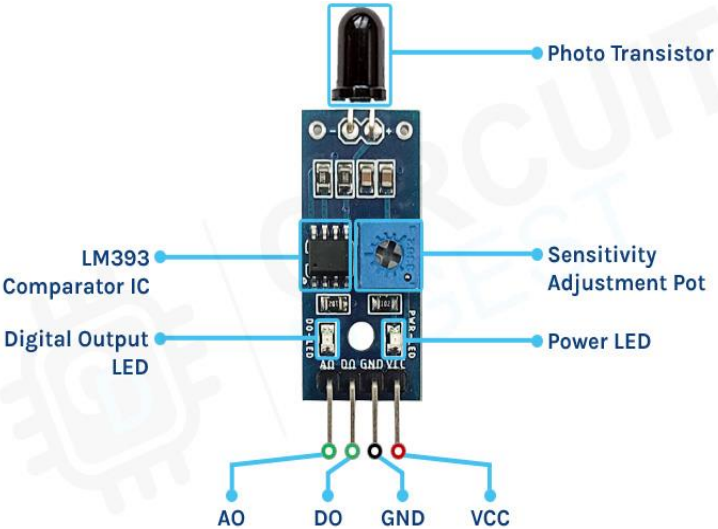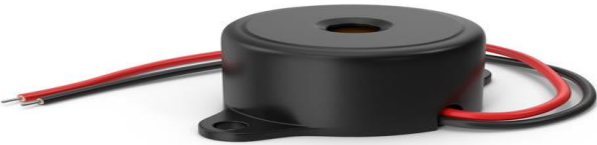3.	Flame Sensor Module A sensor designed to detect infrared radiation emitted by flames, allowing early fire detection.	 The diagram shows a Flame Sensor Module with the following components labeled: - Photo Transistor - LM393 Comparator IC - Sensitivity Adjustment Pot - Digital Output LED - Power LED - AO (Analog Output) - DO (Digital Output) - GND - VCC
4.	Smoke Sensor Module (MQ2) A gas sensor capable of detecting smoke, methane, butane, LPG, and other combustible gases, helping identify fire hazards before they escalate.	 The diagram shows a Smoke Sensor Module (MQ2) with the following components labeled: - Output LED - Power LED - Voltage Comparator IC for Digital Output - Analog Output (AO) - Digital Output (DO) - GND - VCC - Sensitivity Potentiometer - Sensing Element
5.	Buzzer An electronic component that produces a loud alarm sound when smoke or fire is detected, alerting nearby individuals.	 The image shows a black cylindrical buzzer with two wires (red and black) extending from it.

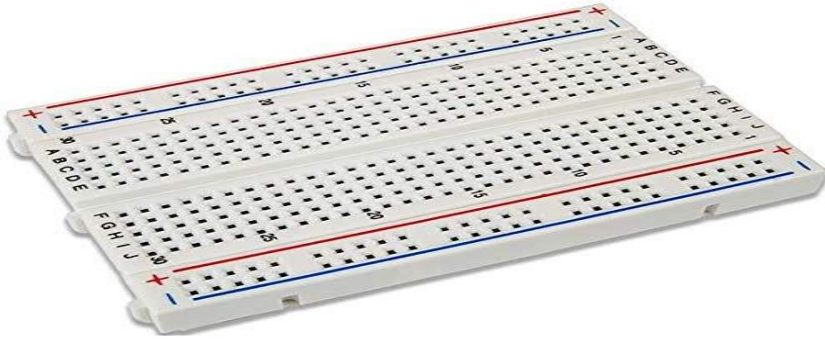6.	Mini Breadboard A solderless prototyping board that allows easy circuit connections between the Arduino, sensors, and other components.	 A white mini breadboard with a grid of holes. It has two rows of holes on each side, labeled A through J. Red and blue lines are printed along the edges, indicating power rails. The board is shown from a slightly elevated angle.
7.	Jumper Wires Electrical connectors used to establish connections between various components, ensuring smooth data flow and circuit functionality.	 Three bundles of jumper wires are shown, each with a different connector type. The first bundle is labeled 'Male + Male' and has two male connectors. The second bundle is labeled 'Female + Male' and has one female and one male connector. The third bundle is labeled 'Female + Female' and has two female connectors. The wires are color-coded in a rainbow pattern (red, orange, yellow, green, blue, purple, brown, black).

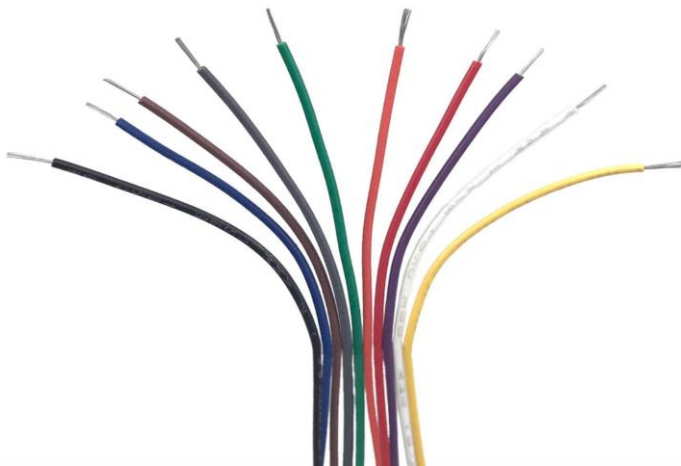8.	Hookup Wires Wires used for stable electrical connections in the circuit, ensuring reliable power and signal transmission.	
9.	Glue Gun with Sticks Used to securely mount sensors and components in place, ensuring a stable and organized setup.	